# **ESE555 VLSI Design**

Assignment 2


Reetam Mandal

114353881


## 4-Input Parity Generator using 3 XOR gates


#### Schematic Design

Single XOR Gate Schematic:

 

### 3-XOR Parity Generator Schematic

 

 

#### **ADE L Simulation**

Supply Voltages 1.1V

External Load 12fF


Rise/Fall times 100ps

To drive the 12fF load, I needed the following parameters:

Bigger/First XOR gates Pmos-width 2um, Nmos-width 1um.length50nm

Last XOR gate Pmos-width 800nm, Nmos-width: 600nm. Length 50nm.

 Inverter:Pmos-width 200nm, Nmos-width:100nm, Length 50nm.



**Propagation Delay= 51ps** 

#### **Power Calculations**



#### Average Current = 11.2nA


Average power consumption is the overall transient current drawn from the supply times the supply voltage:

= I x Vdd


= 1.1V x 11.2 nA

#### Layout

### Single XOR Gate Layout

 


Parity Generator Layout

 


### Area of this Layout is 18.985um X 14.8525um

#### **DRC** Passed

 

LVS Passed

PEX results:

 

#### **Extracted Netlist:**

- \* File: 3XORParityBackupohnonotagain.pex.netlist
- \* Created: Thu Oct 21 20:38:17 2021
- \* Program "Calibre xRC"
- \* Version "v2014.4\_28.20"

\*

.subckt 3XORParityBackupohnonotagain VDD VSS C A D B OUTPUT

\*

mXI5/MM3 XI5/B' D VSS VSS NMOS\_VTL L=5e-08 W=1e-07 AD=1.2e-14 AS=1.2e-14

+ PD=4.4e-07 PS=4.4e-07

mXI5/MM2 XI5/A' C VSS VSS NMOS\_VTL L=5e-08 W=1e-07 AD=1.2e-14 AS=1.2e-14

+ PD=4.4e-07 PS=4.4e-07

mXI2/MM3 XI2/B' B VSS VSS NMOS\_VTL L=5e-08 W=1e-07 AD=1.2e-14 AS=1.2e-14

+ PD=4.4e-07 PS=4.4e-07

mXI2/MM2 XI2/A' A VSS VSS NMOS\_VTL L=5e-08 W=1e-07 AD=1.2e-14 AS=1.2e-14

+ PD=4.4e-07 PS=4.4e-07

mXI5/MM8 NET21 C XI5/NET021 VSS NMOS\_VTL L=5e-08 W=1e-06 AD=1.25e-13 AS=1.25e-13

```
+ PD=2.25e-06 PS=2.25e-06
```

mXI2/MM8 NET22 A XI2/NET021 VSS NMOS\_VTL L=5e-08 W=1e-06 AD=1.25e-13 AS=1.25e-13

+ PD=2.25e-06 PS=2.25e-06

mXI5/MM10 XI5/NET021 D VSS VSS NMOS\_VTL L=5e-08 W=1e-06 AD=1.225e-13 AS=1.35e-13

+ PD=2.245e-06 PS=2.27e-06

mXI2/MM10 XI2/NET021 B VSS VSS NMOS\_VTL L=5e-08 W=1e-06 AD=1.225e-13 AS=1.35e-13

+ PD=2.245e-06 PS=2.27e-06

mXI5/MM9 NET21 XI5/A' XI5/NET28 VSS NMOS\_VTL L=5e-08 W=1e-06 AD=1.3e-13

+ AS=1.2e-13 PD=2.26e-06 PS=2.24e-06

mXI2/MM9 NET22 XI2/A' XI2/NET28 VSS NMOS\_VTL L=5e-08 W=1e-06 AD=1.3e-13

+ AS=1.2e-13 PD=2.26e-06 PS=2.24e-06

mXI5/MM11 XI5/NET28 XI5/B' VSS VSS NMOS\_VTL L=5e-08 W=1e-06 AD=1.225e-13

+ AS=1.25e-13 PD=2.245e-06 PS=2.25e-06

mXI2/MM11 XI2/NET28 XI2/B' VSS VSS NMOS VTL L=5e-08 W=1e-06 AD=1.225e-13

+ AS=1.25e-13 PD=2.245e-06 PS=2.25e-06

mXI6/MM3 XI6/B' NET21 VSS VSS NMOS\_VTL L=5e-08 W=1e-07 AD=1.2e-14 AS=1.2e-14

+ PD=4.4e-07 PS=4.4e-07

mXI6/MM2 XI6/A' NET22 VSS VSS NMOS\_VTL L=5e-08 W=1e-07 AD=1.2e-14 AS=1.2e-14

+ PD=4.4e-07 PS=4.4e-07

mXI6/MM8 OUTPUT NET22 XI6/NET021 VSS NMOS\_VTL L=5e-08 W=6e-07 AD=7.5e-14

+ AS=7.5e-14 PD=1.45e-06 PS=1.45e-06

mXI6/MM10 XI6/NET021 NET21 VSS VSS NMOS\_VTL L=5e-08 W=6e-07 AD=7.35e-14

+ AS=8.1e-14 PD=1.445e-06 PS=1.47e-06

mXI6/MM9 OUTPUT XI6/A' XI6/NET017 VSS NMOS\_VTL L=5e-08 W=6e-07 AD=7.8e-14

+ AS=7.2e-14 PD=1.46e-06 PS=1.44e-06

mXI6/MM11 XI6/NET017 XI6/B' VSS VSS NMOS\_VTL L=5e-08 W=6e-07 AD=7.35e-14

+ AS=7.5e-14 PD=1.445e-06 PS=1.45e-06

mXI5/MM1 XI5/B' D VDD VDD PMOS\_VTL L=5e-08 W=2e-07 AD=2.4e-14 AS=2.4e-14

+ PD=6.4e-07 PS=6.4e-07

mXI5/MM0 XI5/A' C VDD VDD PMOS VTL L=5e-08 W=2e-07 AD=2.4e-14 AS=2.4e-14

+ PD=6.4e-07 PS=6.4e-07

mXI2/MM1 XI2/B' B VDD VDD PMOS VTL L=5e-08 W=2e-07 AD=2.4e-14 AS=2.4e-14

+ PD=6.4e-07 PS=6.4e-07

mXI2/MM0 XI2/A' A VDD VDD PMOS VTL L=5e-08 W=2e-07 AD=2.4e-14 AS=2.4e-14

```
+ PD=6.4e-07 PS=6.4e-07
```

mXI5/MM4 XI5/NET023 C VDD VDD PMOS\_VTL L=5e-08 W=2e-06 AD=2.75e-13 AS=2.65e-13

+ PD=4.275e-06 PS=4.265e-06

mXI2/MM4 XI2/NET023 A VDD VDD PMOS\_VTL L=5e-08 W=2e-06 AD=2.75e-13 AS=2.65e-13

+ PD=4.275e-06 PS=4.265e-06

mXI5/MM6 NET21 XI5/B' XI5/NET023 VDD PMOS\_VTL L=5e-08 W=2e-06 AD=2.9e-13

+ AS=2.55e-13 PD=4.29e-06 PS=4.255e-06

mXI2/MM6 NET22 XI2/B' XI2/NET023 VDD PMOS\_VTL L=5e-08 W=2e-06 AD=2.9e-13

+ AS=2.55e-13 PD=4.29e-06 PS=4.255e-06

mXI5/MM5 XI5/NET022 XI5/A' VDD VDD PMOS\_VTL L=5e-08 W=2e-06 AD=2.75e-13

+ AS=2.8e-13 PD=4.275e-06 PS=4.28e-06

mXI2/MM5 XI2/NET022 XI2/A' VDD VDD PMOS\_VTL L=5e-08 W=2e-06 AD=2.75e-13

+ AS=2.8e-13 PD=4.275e-06 PS=4.28e-06

mXI5/MM7 NET21 D XI5/NET022 VDD PMOS VTL L=5e-08 W=2e-06 AD=2.65e-13 AS=2.4e-13

+ PD=4.265e-06 PS=4.24e-06

mXI2/MM7 NET22 B XI2/NET022 VDD PMOS\_VTL L=5e-08 W=2e-06 AD=2.65e-13 AS=2.4e-13

+ PD=4.265e-06 PS=4.24e-06

mXI6/MM1 XI6/B' NET21 VDD VDD PMOS\_VTL L=5e-08 W=2e-07 AD=2.4e-14 AS=2.4e-14

+ PD=6.4e-07 PS=6.4e-07

mXI6/MM0 XI6/A' NET22 VDD VDD PMOS\_VTL L=5e-08 W=2e-07 AD=2.4e-14 AS=2.4e-14

+ PD=6.4e-07 PS=6.4e-07

mXI6/MM4 XI6/NET023 NET22 VDD VDD PMOS\_VTL L=5e-08 W=8e-07 AD=1.1e-13

+ AS=1.06e-13 PD=1.875e-06 PS=1.865e-06

mXI6/MM6 OUTPUT XI6/B' XI6/NET023 VDD PMOS\_VTL L=5e-08 W=8e-07 AD=1.16e-13

+ AS=1.02e-13 PD=1.89e-06 PS=1.855e-06

mXI6/MM5 XI6/NET015 XI6/A' VDD VDD PMOS\_VTL L=5e-08 W=8e-07 AD=1.1e-13

+ AS=1.12e-13 PD=1.875e-06 PS=1.88e-06

mXI6/MM7 OUTPUT NET21 XI6/NET015 VDD PMOS\_VTL L=5e-08 W=8e-07 AD=1.06e-13

+ AS=9.6e-14 PD=1.865e-06 PS=1.84e-06

c 21 VDD 0 5.78242f

c 42 VSS 0 3.71267f

c 48 XI5/NET021 0 0.148003f

c 54 XI2/NET021 0 0.148003f

c 71 NET22 0 1.54579f

c\_88 NET21 0 2.10363f c\_94 XI6/NET021 0 0.148003f c\_103 C 0 0.524077f c\_112 A 0 0.524077f c\_120 XI5/A' 0 0.720316f c\_128 XI2/A' 0 0.720488f c\_138 XI5/B' 0 0.761227f c\_148 XI2/B' 0 0.761423f c\_153 XI5/NET023 0 0.206638f c\_158 XI2/NET023 0 0.206638f c\_163 XI5/NET022 0 0.227626f c\_168 XI2/NET022 0 0.227626f c\_174 XI5/NET28 0 0.193542f c\_180 XI2/NET28 0 0.193918f c\_189 D 0 1.07594f c\_198 B 0 1.05263f c\_206 XI6/A' 0 0.719385f c\_216 XI6/B' 0 0.75884f c\_221 XI6/NET023 0 0.206638f c\_226 XI6/NET015 0 0.227626f c\_232 XI6/NET017 0 0.193918f c\_243 OUTPUT 0 0.516443f  $. include \ "3XORParityBackupohnonotagain.pex.net list. 3XORPARITYBACKUPOHNONOTAGAIN.pxi" \\$ .ends